

Exp No: 2  
21/8/25

## Analysis of first order R-L & R-C Circuits


Aim: TO study the response of the first order RL and RC circuits.

Apparatus :


AFO

Decade Resistance box	1 No
Decade inductance box	1 No
Decade capacitance box	1 No
Standard Resistance box	1 No
DSO	1 No

Circuit diagram:

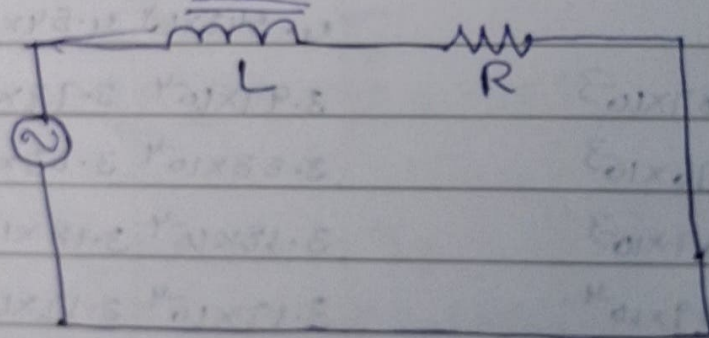





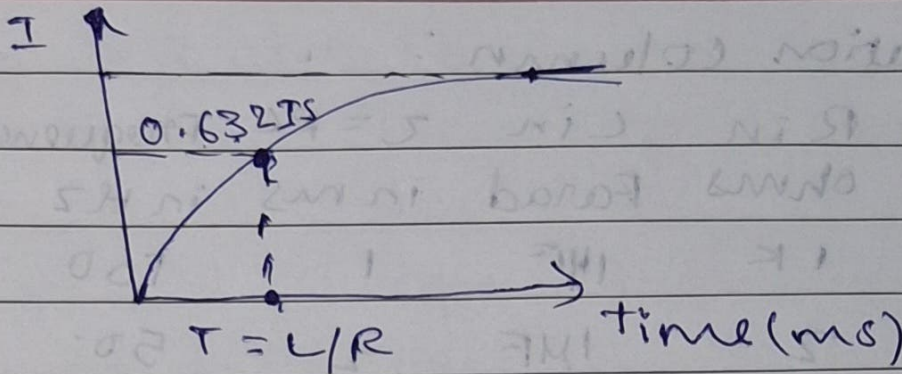

$$\frac{1}{10\tau} = \frac{1}{10 \times \frac{1}{2} \times 10^{-2}}$$

Tabulation column

Sl. No.	$R$ in ohm	$L$ in Henry	$\tau = L/R$ in ms	Frequency measured in Hz	$\tau$ in ms
1	1K	1H	1	100	1.3
2	2K	2H	0.5	<del>200</del>	<del>0.75</del>

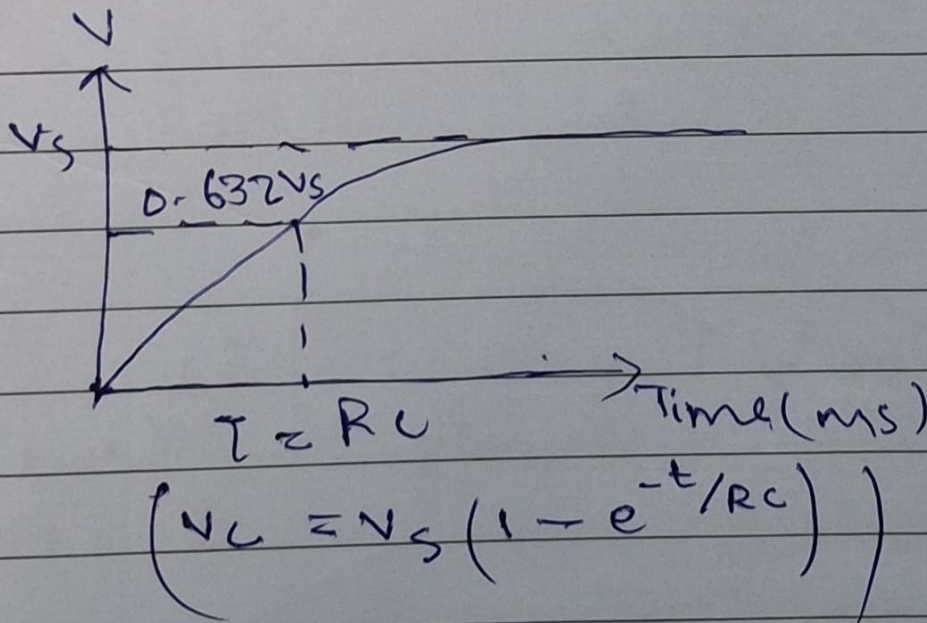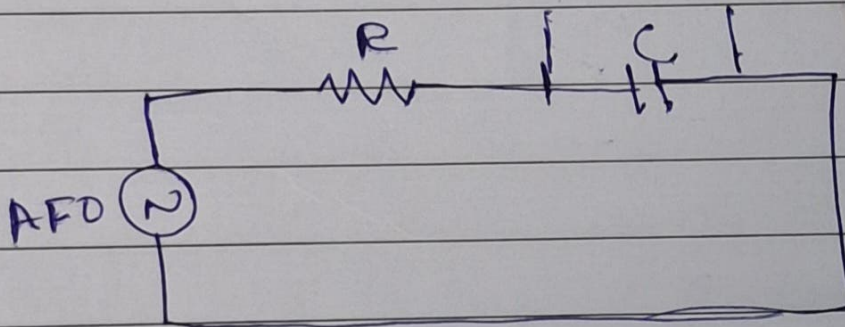



Tabulation column:

Sl. No.	R in ohms	C in Farad	$Z = RC$ in ms	Frequency in Hz	Time constant $Z$ in ms
1	1 K	1 $\mu F$	1	100	1.3
2	2	1 $\mu F$	2	50	2.3

-2 M for  
submitting  
graphs

C-5

V-4



